

(3 Hours)

[Total Marks: 80]


N.B.: (1) Question No. 1 is **Compulsory**.

(2) Attempt any **three** questions out of the remaining **five**.

(3) Each question carries 20 marks and sub-question carry equal marks.

(4) Assume suitable data if required.

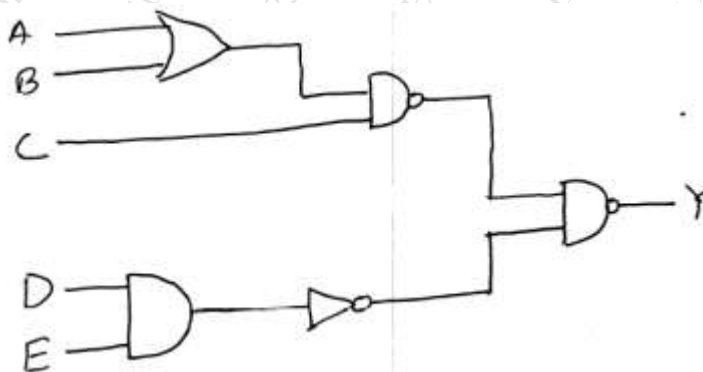1. (a) Convert JK F/F to T F/F (5)
- (b) Explain current and voltage parameters of logic families. (5)
- (c) Design half adder circuit using gates. (5)
- (d) Prove the following Boolean theorem. $(A+\bar{A}B) = (A+B)$ (5)
2. (a) Explain Race around condition in JK F/F and explain how to avoid this condition. (10)
- (b) Convert $(27)_{10}$ & $(42)_{10}$ into binary, octal, hexadecimal, Excess-3 code and gray code. (10)
3. (a) Implement the following expression using 8:1 multiplexer. (10)
 $F(A, B, C, D) = \sum m(2, 4, 6, 7, 9, 11, 14)$
- (b) What is shift register? Explain any one type of shift register in detail. Give its applications. (10)
4. (a) Implement and explain 4 bit BCD adder using IC 7483 (10)
- (b) Design 3 bit synchronous counter using T F/F. (10)
- 5 (a) Find expression of Y for above logic diagram. (10)



- (b) Design 4 bit binary to Gray code converter (10)
6. (a) Explain following characteristics of logic families; (10)
 1. Propagation delay
 2. Noise margin
 3. Power Dissipation
 4. Fan out
 5. Figure of Merit
- (b) Draw K-map for following expression and implement using only Basic gates. (10)
 $F(A, B, C, D) = \sum m(0, 3, 6, 9, 10, 12, 14, 15)$