

(3 Hours)

Total Marks: 80


Note:

- Question No. 1 is compulsory.
- Answer any **three** from the remaining five questions.
- Assume suitable data if necessary and justify the same.

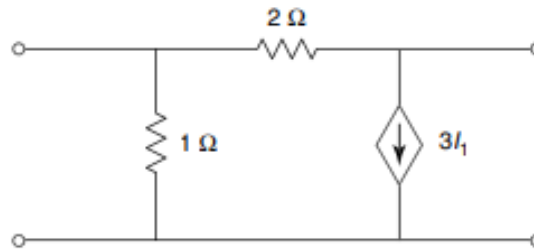Q1 Each question carries five marks


20M

a The open-circuit impedance matrix of the two-port network shown is




b The voltage $V(s)$ of a network is given by $V(s) = \frac{3s}{(s+2)(s^2+2s+2)}$ Plot its pole-zero diagram

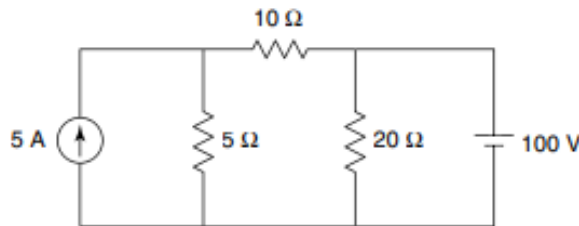c Determine the current through the 20 ohm in the following circuit



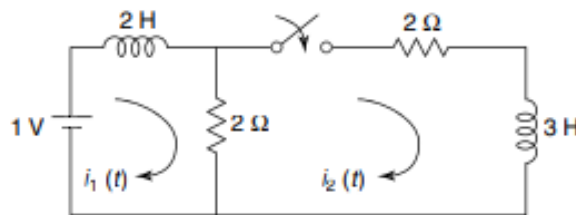d In the network shown, the switch is closed at $t = 0$, the steady-state being reached before $t=0$. Determine the current $i_1(0^+)$ and $i_2(0^+)$.



Q2 a The reduced incidence matrix of an oriented graph is

10M


$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(a) Draw the graph. (b) How many trees are possible for this graph? (c) Write the tieset and cutset matrices.


b Derive the condition for reciprocity and symmetry for ABCD-parameters.

10M

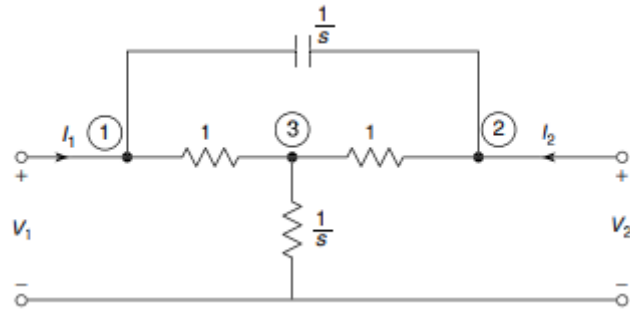
Q3 a Obtain Y-parameters of the network shown 10M



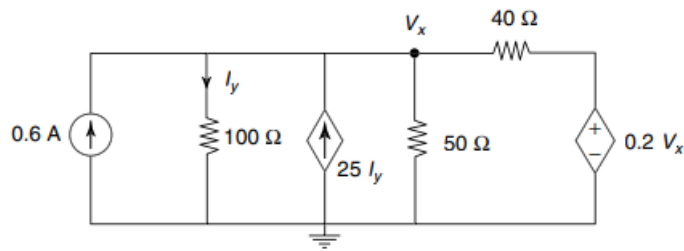
b Find the voltage V_x for the given network using nodal analysis. 10M



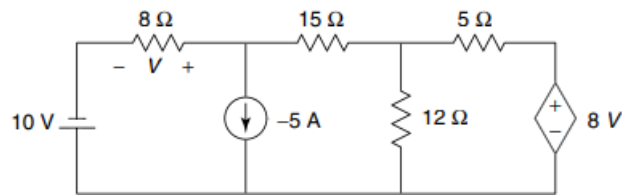
Q4 a Find the voltage V using superposition theorem. 10M



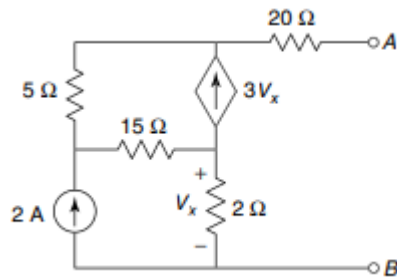
b For the given network, find Norton's equivalent network. 10M



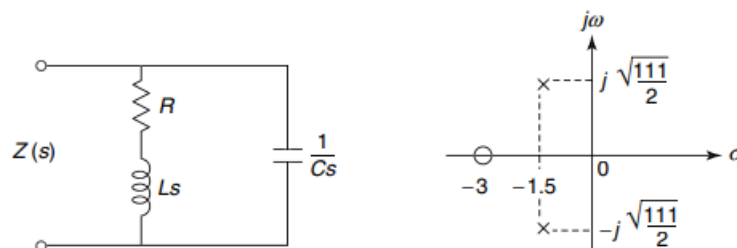
Q5 a A network and its pole-zero configuration are shown as follows. Determine the values of R , L and C if $Z(j0) = 1$. 10M



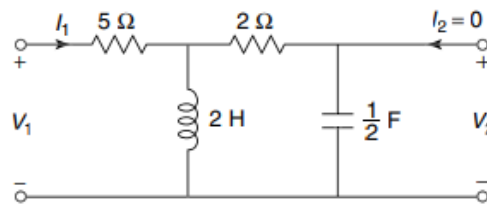- b Determine the driving-point impedance $\frac{V_1}{I_1}$, transfer impedance $\frac{V_2}{I_1}$, and voltage transfer ratio $\frac{V_2}{V_1}$, for the network shown **10M**



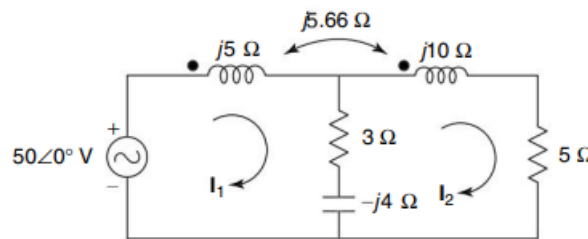- Q6 a Determine the voltage across the 5Ω resistor using mesh analysis. **10M**



- b For the following network, steady state is reached with the switch closed. The switch is opened at $t = 0$. Obtain expressions for $i_L(t)$ and $v_L(t)$. **10M**

