

[Time:3 Hours]

[Total Marks: 80]

**Instructions:**

1. Question No: 1 is compulsory.
2. Answer any **three** of the remaining five questions.
3. Answers to questions should be grouped and written together.

- |          |  |                |
|----------|--|----------------|
| <b>1</b> | Attempt any <b>four</b> of the following:  | <b>(5 x 4)</b> |
|          | a) What is the need for biasing in BJT amplifiers?   |                |
|          | b) Draw and explain the transfer characteristics of n-channel depletion type MOSFET.   |                |
|          | c) Explain the diode as a positive shunt clipper.  |                |
|          | d) Explain the working of op-amp as a zero crossing detector.  |                |
|          | e) Discuss the working of the Zener diode as a voltage regulator.  |                |
| <b>2</b> | a) Determine $I_{CEQ}$ and $V_{CEQ}$ for a voltage divider bias circuit having $V_{CC}=16$ V, $R_1 = 90K\Omega$ , $R_2 = 10K\Omega$ , $R_C = 2.2K\Omega$ , $R_E = 0.68K\Omega$ , $\beta = 210$ . | <b>(10)</b>    |
|          | b) Explain the construction and working of n-channel depletion MOSFET with a neat diagram.   | <b>(10)</b>    |
| <b>3</b> | a) Explain op-amp as a Schmitt trigger circuit. Draw the hysteresis curve.   | <b>(10)</b>    |
|          | b) Draw the hybrid equivalent model for an emitter bias CE amplifier and derive the expression for voltage gain.   | <b>(10)</b>    |
| <b>4</b> | a) What are the different DC biasing techniques used for MOSFET? Analyze any two methods in detail.  | <b>(10)</b>    |
|          | b) Explain the construction and working of the Schottky diode.   | <b>(10)</b>    |
| <b>5</b> | a) Analyse full wave bridge rectifier circuit with LC filter. Draw necessary waveforms.  | <b>(10)</b>    |
|          | b) Explain op-amp as inverting summer circuit.   | <b>(10)</b>    |
| <b>6</b> | a) Illustrate the working of IC555 as an Astable multivibrator.  | <b>(10)</b>    |
|          | b) Discuss the working of the LM317 voltage regulator IC.  | <b>(10)</b>    |

-----