

Time: 3 Hrs

Marks: 80

Note:

1. Question No.1 is compulsory.
2. Attempt any three from the remaining questions.
3. Assume suitable data if applicable.
4. Figures on the right hand side indicate full marks.

- Q.1 Answer **any four** **20 Marks**
- (i) Explain the various shielding techniques in EMC with diagrams
  - (ii) Draw and Compare Maximally flat low pass prototype and Equal ripple low pass prototype, in filter design
  - (iii) What is DFS? Explain the term with a block diagram
  - (iv) What is unilateral figure of merit? Explain its relevance with amplifier design
  - (v) What is the difference between Filter transformation and filter implementation?
- Q.2 a. Explain various coupling modes in EMI **10 Marks**
- b. What is stability parameter in context with Amplifier Design? Explain types of stability and stability circles **10 Marks**
- Q.3 a. Explain the Image parameter method of filter design and mention its characteristics and advantages. **10 Marks**
- b. Derive the expression for available and transducer power gain **10 Marks**
- Q.4 a. Compare various types of Balanced mixers, Image reject mixers **10 Marks**
- b. Explain the concept of Fixed and Variable-Modulus Dividers in Frequency Synthesizers **10 Marks**
- Q.5 a. With an example explain the difference between Maximum Amplifier and Low Noise Amplifier Design steps **10 Marks**
- b. Compare CISPR and FCC standards **10 Marks**
- Q.6 Write a Short Note on **Any two** **20 Marks**
- a) Grounding schemes in EMC
  - b) One-port and two-port microwave oscillator design.
  - c) DDFS