

Duration: 3hrs

[Max Marks:80]

- N.B. : (1) Question No 1 is Compulsory.
(2) Attempt any three questions out of the remaining five.
(3) All questions carry equal marks.
(4) Assume suitable data, if required and state it clearly.

- 1** Attempt any FOUR **[20]**
- a Discuss the selection criteria for switching Power Devices for an application.
 - b Differentiate Micro Grid and Smart Grid..
 - c Explain the Principle of operation of Flyback Converter.
 - d Discuss the need of Multilevel inverters.
 - e Explain Principle of operation of permanent magnet synchronous motor.
- 2** a Explain the working of Buck-Boost converter with waveforms. **[10]**
b Describe the Voltage and frequency control technique for Induction motor. **[10]**
- 3** a Discuss the state space average modelling of DC-DC Buck converter in detail. **[10]**
b Explain PID Control of DC-DC Converter. Also discuss the closed loop stability. **[10]**
- 4** a Explain Grid interface of Renewable energy sources with suitable Block diagram. Also explain the need of synchronization with grid. **[10]**
b Draw and explain speed control of DC motor Drive. **[10]**
- 5** a Explain concept of distributed generation system with Block diagram. **[10]**
b Explain the concept of zero-order-hold (ZOH). Explain the same in detail. **[10]**
- 6** a Illustrate the instantaneous power theory in control of inverters **[10]**
b Discuss methods of parallel operation of inverters with suitable example. **[10]**
-