

S-E. ELEC NEP June 2026

SEM III

(2 Hours)


Total Marks: 60

04/06/26


- Note: 1. Question No. 1 is compulsory.
 2. Answer any THREE from the remaining FIVE questions.
 3. Assume suitable data if necessary and justify the same.
 4. Figure to right indicates marks

Q.1 Attempt any five questions [compulsory problem]

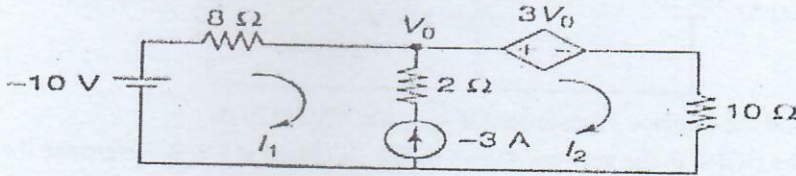
- (a) Find the Laplace Transform of $e^{2t} + 4t^3 - \sin 2t \cdot \cos 3t$ 3
 (b) Determine the constants a, b, c, d if $f(z) = (x^2 + 2axy + by^2) + i(cx^2 + 2dxy + y^2)$ is analytic. 3
 (c) In the network of following Fig. find currents I_1 and I_2 . 3



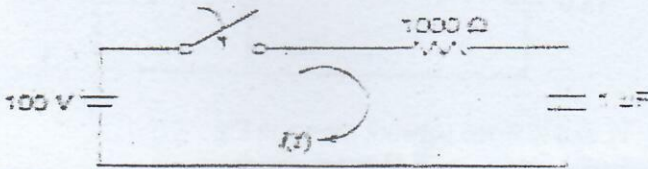
- (d) Define the term "Loop" and write its properties? 3
 (e) In the network of Fig. the switch is closed at $t = 0$. With the capacitor uncharged, find value for i at $t = 0^+$. 3



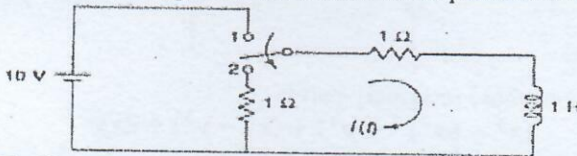
- (f) Define Unit step Function and find its Laplace Transform. 3
 Q.2 (a) Find $L(e^{-3t} \cosh 5t \cdot \sin 4t)$ 4
 (b) In the network of Fig, the switch is moved from the position 1 to 2 at $t = 0$, steady-state condition having been established in the position 1. Determine $i(t)$ for $t > 0$. 5



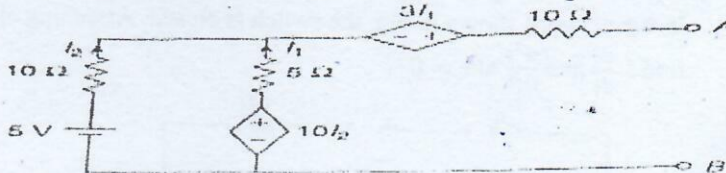
- (c) Find Norton's equivalent network across terminals A and B of Fig. 6



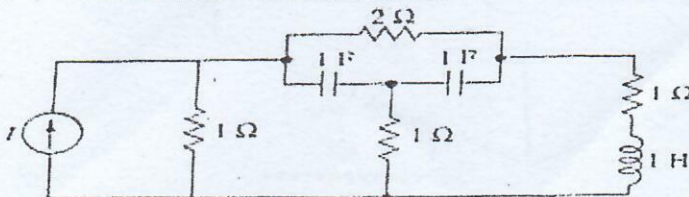
- Q.3 (a) Construct an analytic function whose real part $e^x \cos y$ 4
 (b) Find The Inverse Laplace Transforms Of $\frac{s+29}{(s+4)(s^2+9)}$ 5
 (c) For the circuit shown in Fig. (i) draw its graph, (ii) draw its tree, and (iii) write the fundamental cutset matrix. 6



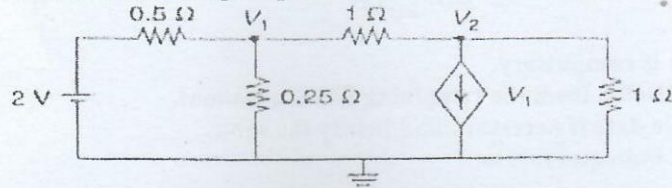- Q.4 (a) Determine the voltages V_1 and V_2 in the network of Fig.




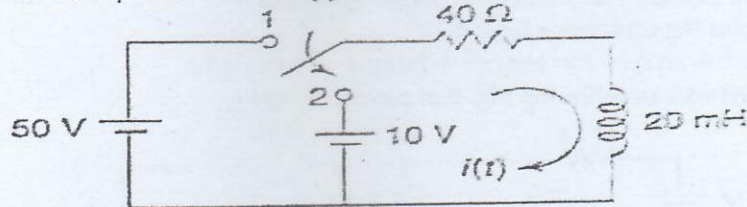- (b) The network of Fig. is under steady state with switch at the position 1. At $t = 0$, switch is moved to position 2. Find $i(t)$.




- (c) Find the Laplace Transforms Of $\int_0^t u e^{-3u} \cos^2 2u \, du$

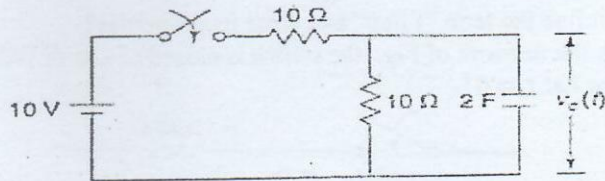- Q.5 (a) The switch in the network shown in Fig. is closed at $t = 0$. Determine the voltage across the capacitor.



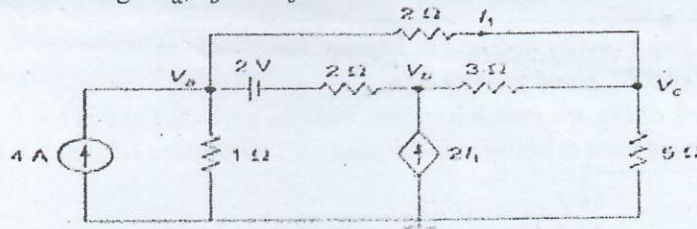
- (b) Find voltages V_a , V_b and V_c in the network shown in Fig.



- (c) Find the analytic function whose imaginary part is $(x^4 - 6x^2y^2 + y^4) + (x^2 - y^2) + 2xy$

- Q.6 (a) Find k such that $\frac{1}{2} \log(x^2 + y^2) + i \frac{kx}{y}$ is analytic.

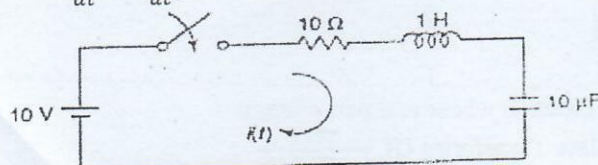- (b) In the network shown in Fig. the switch is closed. Assuming all initial conditions as zero, find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$.



- (c) Draw the dual of the network of Fig.

