

BE SEM VIII C choice based) Summer 2026 EXTC

Time: 3 Hours

Maximum Marks: 80

1415126

- NB. 1. Question number one is compulsory
 2. Attempt any three out of remaining five questions
 3. Assume suitable data wherever required
 4. Figures to the right indicate the maximum marks

Q1: Attempt any four

- i) Draw and Compare Maximally flat low pass prototype and Equal ripple low pass prototype, in filter design. (5)
- ii) Why is value of $m=0.6$ in matching section of filter in design by image parameter method. (5)
- iii) Explain 1 dB compression in power amplifier designing (5)
- iv) Give the characteristics of mixers. (5)
- v) What are various types of gains defined in RF Amplifiers? (5)

- Q2: A) Give the significance of each section in Image parameter method of filter design. (10)
 B) Derive the expression for available power gain G_A . (10)

- Q3: A) Silicon bipolar junction transistor has the following scattering parameters at 1 GHz
 $S_{11} = 0.38 \angle -158^\circ$, $S_{12} = 0.11 \angle 54^\circ$, $S_{21} = 3.5 \angle 80^\circ$, $S_{22} = 0.40 \angle -43^\circ$. The source impedance $Z_s = 25\Omega$ and load impedance $Z_L = 40\Omega$. Compute the Power gain, the overall power gain and transducer power gain. (10)
 B) Compare various types of Diode and FET Mixers (10)

- Q4: A) Explain various coupling modes in EMI (10)
 B) Explain Bonding and Shielding in EMC (10)

- Q5: A) Show that reflection coefficient is larger than 1 for negative load resistance. (10)
 Why negative resistance is important in oscillator design.
 B) Discuss, in detail, the role of ANSI standards in EMI/EMC area. (10)

- Q6: A) Short note on microwave filter implementation (10)
 B) Write short note on Richard's Transformation (10)