

Duration: 3hrs

Total Marks:80

- N.B.:** (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

- 1** Attempt any **FOUR** [20]
- a Convert $(1110010.1010)_2 = (?)_{16} (?)_8 (?)_{10} (?)_{\text{gray}} (?)_{\text{XS-3code}}$ [5]
- b Implement 8:1 Mux with 4:1 Mux [5]
- c What is latch? How a latch is different from flip flop? [5]
- d Compare SRAM and DRAM [5]
- e Compare PLA and PAL [5]
- 2** a $F(p,q,r,s) = \sum m(0,2,5,6,8,9,11,13) + d(3,7,15)$ solve using K-map [10]
- b Explain the sample and hold circuit. [10]
- 3** a Explain the MasterSlave JK flipflop. [10]
- b Explain the classification and characteristics of memory. [10]
- 4** a Design the 4 bit Asynchronous counter. [10]
- b Implement 3 bit binary to gray converter using NAND gate [10]
- 5** a What is universal shift register ? Draw the circuit and explain its working. [10]
- b Explain the 3 bit R-2R D/A converter [10]
- 6** a Implement the T to D flip flop and JK to SR [10]
- b Short on any two: [10]
- i) Dual slop A to D converter
- ii) FPGA
- iii) Shift Register